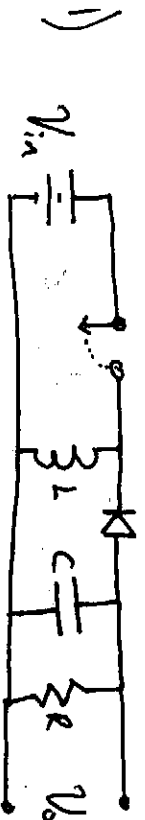


6.331 Set 4 Josh Gordonson



$$L = 150 \mu\text{H}$$

$$C = 820 \mu\text{F}$$

$$R = 50 \Omega$$

a)

$$\Delta I_{L,eq} = \Delta I_{L,q} \quad \text{in steady state}$$

$$V_L = L \frac{dI_L(t)}{dt} \rightarrow I_L(t) = \int \frac{V_L}{L} dt \rightarrow \Delta I_{L,open} = \int_0^{bT} \frac{V_L}{L} dt = \frac{V_L bT}{L} = \frac{V_{in} bT}{L}$$

$$-\Delta I_{L,closed} = \Delta I_{L,open} \rightarrow$$

$$\boxed{\frac{V_{out}}{V_{in}} = \frac{-b}{1-b}}$$


$$\Delta I_{L,closed} = \int_{bT}^T \frac{V_L}{L} dt = \frac{V_{out} (1-b)T}{L}$$

Up Converter: $b > 0.5 \rightarrow \left| \frac{V_o}{V_i} \right| > 1$ Down Converter: $b < 0.5 \rightarrow \left| \frac{V_o}{V_i} \right| < 1$

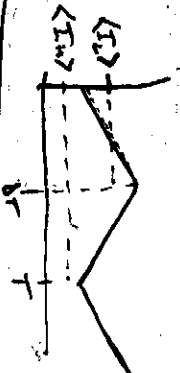b) $\langle I_{in} \rangle = \langle I_{out} \rangle$

$$V_{in} \langle I_{in} \rangle = \frac{\langle V_{out} \rangle^2}{R}$$

$$\langle I_{in} \rangle = \frac{\langle V_{out} \rangle^2}{V_{in} R}$$




$$\boxed{\Delta V_{out} = \Delta V_{out,open} = \frac{\langle V_{out} \rangle}{RC} bT = 200 \text{ mV}}$$

$$\langle I_L \rangle = \frac{50^2}{75 \cdot 50 \cdot 0.01} = \frac{2}{3} \cdot \frac{1}{4} = 1.6 \text{ A}$$

$$\langle I_{in} \rangle = .6 \text{ A}$$
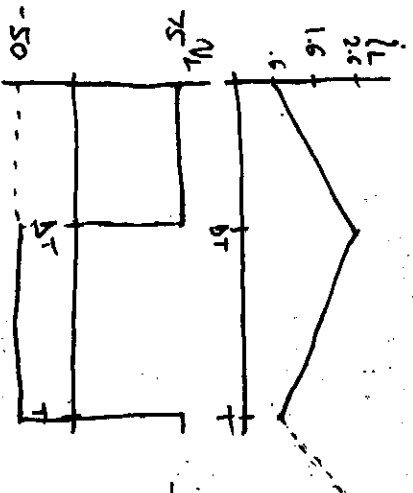
$$\langle V_{out} \rangle = 50 \text{ V}$$



c)

~~1~~

$$L \frac{d \langle i_L \rangle}{dt} = \langle V_L \rangle = D V_i + (1-D) \langle V_C \rangle$$

$$C \frac{d \langle V_C \rangle}{dt} = \langle I_d \rangle - \frac{\langle V_C \rangle}{R_L} = (1-D) \langle i_L \rangle - \frac{\langle V_C \rangle}{R_L}$$

$$C \frac{d^2 \langle V_C \rangle}{dt^2} = \frac{d \langle i_L \rangle}{dt} - \frac{d \langle V_C \rangle}{dt} - D \frac{d \langle i_L \rangle}{dt} - \frac{1}{R_L} \frac{d \langle V_C \rangle}{dt}$$

$$C \frac{d^2 \langle V_C \rangle}{dt^2} = \left(\frac{1-D}{L} \right) (D V_i + (1-D) \langle V_C \rangle) - \frac{d \langle V_C \rangle}{dt} - \frac{1}{R_L} \frac{d \langle V_C \rangle}{dt}$$

$$\frac{d^2 \langle V_C \rangle}{dt^2} + \frac{1}{RC} \frac{d \langle V_C \rangle}{dt} + \frac{(1-D)^2}{LC} \langle V_C \rangle = \frac{D(1-D)}{LC} V_{in} - \frac{\langle i_L \rangle}{C} \frac{dD}{dt}$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{d V_C}{dt} + \frac{(1-D)^2}{LC} (V_C + V_C) = \frac{(D+D)(1-D-D)}{LC} V_{in} - \frac{(I_L + i_L)}{C} \frac{d}{dt}$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{d V_C}{dt} + \frac{(1-D)^2}{LC} (V_C + V_C) = \frac{2D(1-D)}{LC} V_C =$$

$$+ \frac{D(1-D)}{LC} V_{in} + \frac{d(1-2D)}{LC} V_{in} - \frac{I_L}{C} \frac{dD}{dt}$$

$\langle V_C \rangle = V_C + V_C$
 $D = D + d$
 $\langle i_L \rangle = I_L + i_L$
 ignore 2nd order terms
 don't care about i_L
 $R_L I_L + d^2 - D + d - d + d - d + d$
 $= (1-D)^2 - 2d(1-D)$
 $= D^2 - 2D + d^2 + d - d - d^2$
 $= D^2 + d - 2D + d$
 $V_0 = V_C = \frac{-D}{1-D}$
 $V_C = \frac{-D V_C}{(1-D)}$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{d V_C}{dt} + \frac{(1-D)^2}{LC} V_C = \frac{2d(1-D)}{LC} V_C + \frac{D(1-D)}{LC} V_{in} + \frac{d(1-2D)}{LC} V_{in} - \frac{I_L}{C} \frac{dD}{dt}$$

$$\frac{V_C(s)}{D(s)} =$$

$$\frac{2(1-D)(-D V_{in})}{LC} + \frac{(1-2D) V_{in}}{LC} - \frac{I_L s}{C} =$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{RC} \frac{d V_C}{dt} + \frac{(1-D)^2}{LC} V_C = \frac{2d(1-D)}{LC} V_C + \frac{D(1-D)}{LC} V_{in} + \frac{d(1-2D)}{LC} V_{in} - \frac{I_L}{C} \frac{dD}{dt}$$

$$\frac{V_C(s)}{D(s)} =$$

$$\frac{1 \frac{D}{LC} V_{in} - \frac{I_L s}{C}}{s^2 + \frac{1}{RC} s - \frac{(1-D)^2}{LC}} = \left[\frac{V_{in} - \frac{I_L s}{C}}{\frac{1}{LC} s^2 - \frac{I_L s}{C}} \right]$$

→ RHP zero, identical to Boost Converter Transfer function.


b)

$$R_{01} = 1\Omega \quad V_b = 0.35V + 0.1\Omega i_b$$

$$\langle P_{5w} \rangle = 5 \frac{V_b^2}{R} = 5 i_b^2 R = 5 (1.6A)^2 \cdot 1\Omega = 1.025W$$

$$\langle P_{load} \rangle = V_b i_b = (0.35V + 0.1\Omega \cdot i_b) i_b \rightarrow \frac{d}{dt} \frac{1}{2} i_b^2 \quad (1-b) \langle I_b \rangle (0.35V + 1\Omega \langle I_{L,2} \rangle) = .44W$$

2)

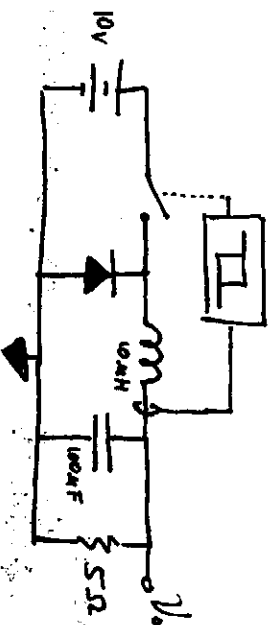

a)

$$\Delta i_{L_{\text{nom}}} = \int_{\frac{T}{2}}^T V_{L_{\text{avg}}} dt = \frac{(1-D)T}{L} V_o$$

$$= \frac{0.5 \cdot 4 \mu\text{s} \cdot 5}{10 \mu\text{H}} = 1 \text{ A}$$

for $f = 250 \text{ kHz}$, $T = 4 \mu\text{s}$

for $\frac{V_o}{V_i} = 0.5$, $D = 0.5$


b)

$V_{\text{out}} = 7.5 \text{ V} \rightarrow D = \frac{7.5}{10} = 0.75$, $\Delta i_L = 1 \text{ A} \rightarrow f = \frac{(1-D)V_o}{L \Delta i_L} = 187.5 \text{ kHz}$

$V_{\text{out}} = 2.5 \text{ V} \rightarrow D = 0.25$, $\Delta i_L = 1 \text{ A} \rightarrow f = \frac{(1-0.25)2.5}{L \Delta i_L} = 187.5 \text{ kHz}$

If $V_{\text{out}} < 2.5 \text{ V}$, $I_{\text{set}} < 0.5 \text{ A}$, and the converter leaves Continuous Conduction mode (CCM) + enters DCM. In DCM, the hysteresis controller ~~loses~~ loses the ability to maintain a 1A Hysteresis band.

c)

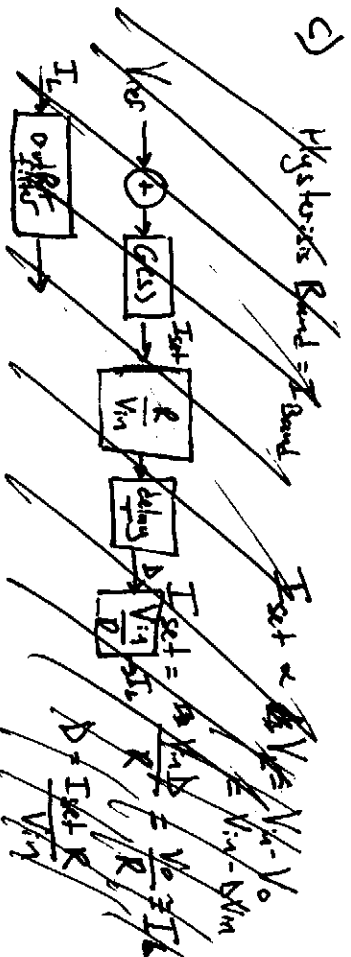


$$Z(R||C) \Rightarrow \frac{R}{RCs+1}$$

$$\frac{V_o}{I_{\text{set}}} = e^{-\frac{sT}{RCs+1}} = e^{-\frac{s(4 \times 10^{-5})}{0.5 \times 10^{-3}s+1}}$$

$$L(s) = G(s) \frac{V_o}{I_{\text{set}}}(s) = G(s) e^{-\frac{sT}{RCs+1}} \Rightarrow$$

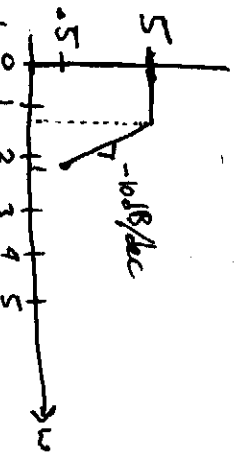$\hookrightarrow G(s)$ needs an integrator, gain, + maybe a zero.



$$G(s) = \frac{5 \times 10^{-1} s + 1}{5 \cdot 10^{-5} s}$$

$$\rightarrow L(s) = \frac{e^{-s(4 \times 10^{-5})}}{10^{-5} s}$$

$$\angle L(j10^5) = -90^\circ - 220^\circ = -112^\circ$$

2b)




$$\text{R || } R + \frac{1}{Cs} = \frac{R + \frac{R}{Cs}}{R + R + \frac{1}{Cs}} = \frac{R + \frac{R}{Cs}}{2R + \frac{1}{Cs} + 1}$$

$$L(s) = \frac{e^{-s(4 \times 10^{-6})} \cdot (10^{-5}s + 1)(5 \times 10^{-4}s + 1)}{10^{-5}(\cancel{5 \times 10^{-4}s + 1})s(5.1 \times 10^{-4}s + 1)}$$

You throw in another zero + move the pole that you are trying to cancel.

Though, this isn't much of a problem:

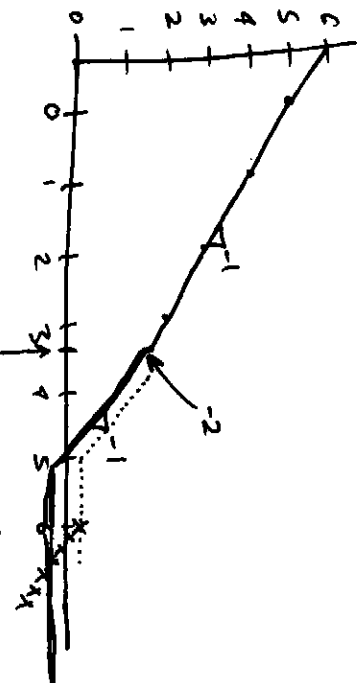


Pole-zero doublet separated by ESR resistance causes us to cross over only slightly earlier. (0.98×10^5 instead of 10^5)

So we can ignore this if we put the zero before that pole \rightarrow put the zero at $\frac{1}{5.1 \times 10^4}$ Hz. Then, put another pole a decade after crossover to make sure that we will cross over at some point.

$$G'(s) = \frac{5.1 \times 10^{-4}s + 1}{5 \cdot 10^{-5}s(10^{-6}s + 1)}$$

3) a)

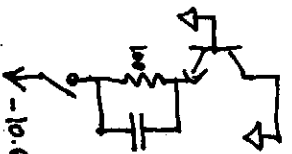

$\beta_F = 100$ $R_E = 5$ $\tau_F = 0.5 \text{ ns}$ $\tau_{BF} = 1 \text{ ns}$ $\tau_S = 7.55 \text{ ns}$

~~$V_E = i_C (100k) + (-10.6V) = 10.6V$~~

$$-i_C = \frac{10V}{100k} = 0.1 \text{ mA} \quad i_C(t) = I_F \left(\frac{1}{\tau_F} + \frac{1}{\tau_{BF}} \right) + \frac{dI_F}{dt}$$

$$i_C = \frac{I_F(t)}{\tau_F} \approx 0.1 (1 - e^{-2.02 \times 10^9 t})$$

$$I_F(t) = \left(\frac{\tau_F \tau_{BF}}{\tau_F + \tau_{BF}} \right) \cdot 0.1 \text{ mA} (1 - e^{-\frac{t}{\tau_F + \tau_{BF}}}) = 4.9 \times 10^{-11} (1 - e^{-2.02 \times 10^9 t})$$

5)

$$-i_C = \frac{10V}{100k} \mu(t) + i_{Ceq} = 0.1 \text{ mA} \mu(t) + C \cdot 10V \delta(t)$$

$$\tau = \frac{\tau_F \tau_{BF}}{\tau_F + \tau_{BF}} = 4.95 \times 10^{-10}$$

~~$i_C = i_{Ceq} + i_{Ceq}$~~

$$-i_C = I_F(t) \left(\frac{1}{\tau_F} + \frac{1}{\tau_{BF}} \right) + \frac{dI_F}{dt}$$


$$I_F(t) = \tau (0.1 \text{ mA}) (1 - e^{-t/\tau}) + C \cdot 10V e^{-t/\tau}$$

$$10C = \tau (0.1 \text{ mA})$$

$$C = \frac{0.1 \tau_F}{10} = \frac{\tau}{100} \approx 5 \text{ pF}$$

$$i_C = \frac{I_F(t)}{\tau_F} = 0.1 \text{ mA} (1 - e^{-2.02 \times 10^9 t}) + 5 \times 10^{-11} e^{-\frac{t}{\tau}}$$

c)

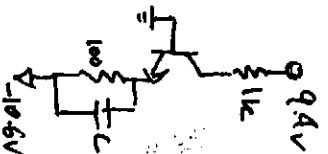

$$-i_C = \frac{10V}{100k} \mu(t) = 0.1 \text{ mA} \mu(t) = I_F \left(\frac{1}{\tau_F} + \frac{1}{\tau_{BF}} \right) + \frac{dI_F}{dt} \quad \tau = \frac{\tau_F \tau_{BF}}{\tau_F + \tau_{BF}} \approx 5 \times 10^{-10}$$

$$I_F = \tau (0.1 \text{ mA}) (1 - e^{-t/\tau})$$

$$i_C = \frac{I_F(t)}{\tau_F} = \frac{\tau_{BF}}{\tau_F + \tau_{BF}} (0.1 \text{ A}) (1 - e^{-t/\tau})$$

$$V_{CE, \text{sat}} = 0.2 \text{ V}$$

$$V_C = 9.4 \text{ V} - i_C (1k) = 9.4 \text{ V} - \frac{\tau_{BF} \tau_F}{\tau_F + \tau_{BF}} (0.1 \text{ A}) (1 - e^{-t/\tau}) \cdot 1k$$

$$V_{CE, \text{sat}} \approx 9.4 \text{ V} - (0.1 \text{ A}) (1 - e^{-2 \times 10^9 t}) \cdot 1k$$

$$\frac{dV_C}{dt} = \frac{d}{dt} \left(9.4 \text{ V} - \frac{\tau_{BF} \tau_F}{\tau_F + \tau_{BF}} (0.1 \text{ A}) (1 - e^{-t/\tau}) \cdot 1k \right) = -\frac{10V}{100V} \cdot \frac{\tau_F + \tau_{BF}}{\tau_F} \rightarrow t = 5.1 \times 10^{-11}$$

d)

$$I_{B0} = \tau_F I_{C, \text{sat}}$$

$$I_{C, \text{sat}} = \frac{10V}{100k} = 0.1 \text{ mA} \rightarrow I_{B0} = 0.5 \text{ nA} \cdot 10 \text{ mA} = 5 \text{ pC}$$

$$I_{B0} \approx 5 \text{ pC}$$

$$I_{B0} = I_{C, \text{sat}} = 0.1 \text{ mA}$$

D) continued:

I_{Csat} is all you'll get from the collector, so the rest has to come from the base.

Steady State: $I_E = .1A$, $I_C = I_C + I_B$ $I_C = I_{Csat} = 10mA$

$$I_{Bq} = I_C - I_{Csat} + \frac{I_{Csat}}{\beta}$$

$$I_{Bq} = .09A + \frac{.01}{100}$$

Since $i_B = \frac{q_E}{C_F} + \frac{dq_E}{dt} + \frac{q_E}{C_{GE}} + \frac{dq_{GE}}{dt}$

$$i_C = \frac{q_E}{C_F} - \frac{1000}{76t} - q_E \left(\frac{1}{\tau_C} + \frac{1}{\tau_{GE}} \right)$$

$$i_C = i_B + i_C = 100mA$$

$$i_C = 10mA = \frac{q_E}{C_F} - q_E \left(\frac{1}{\tau_C} + \frac{1}{\tau_{GE}} \right) \rightarrow 10mA = \frac{(10mA - \frac{q_E}{C_{GE}}) \tau_{GE}}{\tau_C} - \frac{q_E}{\tau_C} + \frac{q_E}{\tau_{GE}} \rightarrow q_E = \frac{(9 - 0.1) \left(\frac{1}{\tau_C} + \frac{1}{\tau_{GE}} + \frac{100}{\tau_{GE}} \right)}{\frac{1}{\tau_C} + \frac{1}{\tau_{GE}}}$$

$$i_B = 90mA = \frac{q_E}{C_F} + \frac{q_E}{\tau_{GE}} \rightarrow q_E = (90mA - \frac{q_E}{\tau_{GE}}) \tau_{GE}$$

$$q_E = 260pC$$

$$q_R = 921pC$$

$$i_B = 90mA; \quad i_R - I_{B0} = \frac{q_E}{\tau_C} + \frac{dq_E}{dt}$$

$$899mA = \frac{q_E}{\tau_C} \rightarrow q_E = 679pC$$

$$q_F + q_R = q_{R0} + q_E \rightarrow 684 = 684$$

E)

$$-i_C = \frac{10V}{1000} u(t) + i_{Ceq} = 0.1A u(t) + C(10V) \delta(t) = \frac{q_E}{\tau_F} + \frac{q_E}{\tau_{GF}} + \frac{dq_E}{dt}$$

$$q_F = 0.1A \tau_C (1 - e^{-t/\tau_C}) + C(10V) e^{-t/\tau_C}, \quad \tau_C = 500 \times 10^{-12}$$

$$i_C = \frac{q_E}{\tau_F} = 0.1A \frac{\tau_C}{\tau_F} (1 - e^{-t/\tau_C}) + \frac{10C}{\tau_C} e^{-t/\tau_C}$$

Substitute $V_{CE} = 0$, $V_C = -0.6V = q_A - R_E i_C \Rightarrow K(0.1A \frac{\tau_C}{\tau_F} (1 - e^{-t/\tau_C}) + \frac{10C}{\tau_C} e^{-t/\tau_C}) = 10V$

$$\frac{10V}{1000} \cdot \tau_F - \frac{\tau_C}{10} = e^{-t/\tau_C} \left(-\frac{\tau_C}{10} + 10C \right) \quad t = -\tau_C \ln \left(\frac{\frac{10}{1000} \tau_F - \frac{\tau_C}{10}}{10C - \frac{\tau_C}{10}} \right)$$

Solve $t=0$ for a real C, $C = .5pC$

F) $i_C = 0 \rightarrow i_B = i_C = 0.1A$

G)

$$i_B - I_{B0} = \frac{q_E}{\tau_C} + \frac{dq_E}{dt} = -10mA - \frac{10mA}{100} = \frac{q_E}{\tau_C} + \frac{dq_E}{dt}$$

$$q_E(\infty) = -10.1mA \cdot \tau_C = -76pC \quad q_E(t_{SB}) = -76pC + 679pC (e^{-t_{SB}/\tau_C}) = 0$$

$$t_{SB} = \ln \left(\frac{679pC}{76pC} \right) \tau_C = 116.5ns$$

3H)

